

## Amplifier

1. A voltage divider consists of the resistors  $R_1 = 2 \text{ k}\Omega$  and  $R_2 = 20 \text{ k}\Omega$ .
  - a) What is the output voltage taken away from the  $R_1$  resistor if the input voltage is 230 V?
  - b) What is the voltage gain?
  - c) What is the power gain? (Neglect the difference between  $R_{\text{in}}$  and  $R_{\text{out}}$ .)
  - d) What is the power gain level in decibel units?
2. How many kilohms should be the resistance of the  $R_2$  resistor of the voltage divider, if we want to take away 25% of the input voltage from the  $R_1 = 1200 \text{ }\Omega$  resistor?
3. The power gain level of a voltage divider is -23 dB. (Neglect the difference between  $R_{\text{in}}$  and  $R_{\text{out}}$ .)
  - a) What is the power gain?
  - b) What is the voltage gain?
  - c) How many ohms should be the  $R_2$  resistor if the output voltage is taken away from  $R_1 = 1 \text{ k}\Omega$ ?
4. For the voltage divider shown in *Fig. 1*  $U_{\text{in}} = 100 \text{ V}$ ,  $R_1 = 1700 \text{ }\Omega$ ,  $R_2 = 300 \text{ }\Omega$ . Find  $U_{\text{out}}$  and  $A_U$ .
5. For the voltage divider shown in *Fig. 1*  $U_{\text{out}} = 100 \text{ V}$ ,  $R_1 = 1700 \text{ }\Omega$ ,  $R_2 = 300 \text{ }\Omega$ . Find  $U_{\text{in}}$  and  $A_U$ .
6. For the voltage divider shown in *Fig. 1*  $U_{\text{in}} = 250 \text{ V}$ ,  $R_1 = 800 \text{ }\Omega$ ,  $U_{\text{out}} = 75 \text{ V}$ . Find  $R_2$ .
7. For the voltage divider shown in *Fig. 1*  $U_{\text{in}} = 250 \text{ V}$ ,  $R_2 = 800 \text{ }\Omega$ ,  $U_{\text{out}} = 75 \text{ V}$ . Find  $R_1$ .
8. For the voltage divider shown in *Fig. 1*  $A_U = 0.05$  and  $R_2 = 2 \text{ k}\Omega$ . Find  $R_1$ .
9. For the voltage divider shown in *Fig. 1*  $A_U = 0.08$  and  $R_1 = 4 \text{ k}\Omega$ . Find  $R_2$ .
10. The input voltage of the potentiometer shown in *Fig. 2* is 200 V. To what % should the wiper be adjusted so that the output voltage becomes
  - a) 40 V
  - b) 100 V
  - c) 0 V
  - d) 200 V?
11. The input voltage of the potentiometer shown in *Fig. 2* is 10 V. What is the output voltage if the wiper stands at 20%?

*Fig. 1*

*Fig. 2*

12. An amplifier amplifies the amplitude of the input signal voltage by one thousand fold. Find the power gain level. (Suppose  $R_{in} = R_{out}$ .)
13. An amplifier amplifies the signal power by a factor of one thousand. Find
  - a) the voltage gain (suppose  $R_{in} = R_{out}$ ) and
  - b) the power gain level.
14. By how many times does an amplifier of 43 dB amplify the signal power? ( $R_{in} = R_{out}$ )
15. The halving of the signal voltage corresponds to how many decibels change? ( $R_{in} = R_{out}$ )
16. We double the voltage of a signal with an amplifier. What is the change in signal power expressed on the decibel scale? ( $R_{in} = R_{out}$ )
17. How many decibels is the power gain level if the output power belonging to the 2 W input power is
  - a) 2000 W
  - b) 100 W
  - c) 4 W
  - d) 2 W
  - e) 1 W
  - f) 0.2 W
  - g) 0 W?
18. To what power does an amplifier amplify the 5 W input signal power if the power gain level for this signal is
  - a) 50 dB
  - b) 3.7 B
  - c) 10 dB
  - d) 1 dB
  - e) 0 dB
  - f) -1 dB
  - g)  $-\infty$  dB?
19. Two harmonic (i.e. sinusoidal) signals of equal power but different frequencies ( $f_1$  and  $f_2$ ) are amplified with an amplifier the power gain level of which is 30 dB at the  $f_1$  and 27 dB at the  $f_2$  frequency. What is the power ratio of the amplified signals?
20. Two harmonic signals of equal power but different frequencies ( $f_1$  and  $f_2$ ) are amplified with an amplifier the power gain level of which is 50 dB at the  $f_1$  and 33 dB at the  $f_2$  frequency. What is the power ratio of the amplified signals?
21. The power gain level of an amplifier without feedback is 50 dB. What will be the power gain level if 1% of the output signal voltage is fed back in opposite phase? The difference between  $R_{in}$  and  $R_{out}$  can be neglected.
22. The power gain level of an amplifier is 13 dB. It decreases to 10 dB as a result of negative feedback. What part of the output voltage is fed back? The difference between  $R_{in}$  and  $R_{out}$  is to be neglected.
23. The power gain level of an amplifier is 26 dB. It decreases to 20 dB as a result of negative feedback. What percentage of the output voltage is fed back? The difference between  $R_{in}$  and  $R_{out}$  is negligible.

24. The voltage gain of an amplifier is 100 without feedback. 3% of the output voltage is fed back in opposite phase with a feedback loop.  $R_{in}$  and  $R_{out}$  can be considered equal.
- a) What is the power gain level without feedback?
  - b) To what value does the voltage gain change as a result of the feedback?
  - c) What will be the power gain level as a result of the feedback?

## Formulae

$$R = \frac{U}{I} \quad (\text{Ohm's law})$$

$$P = U \cdot I = \frac{U^2}{R} = I^2 \cdot R \quad (\text{electric power})$$

$$\frac{U_1}{U_T} = \frac{R_1}{R_1 + R_2} \quad (\text{voltage divider})$$

$$A_U = \frac{U_{ki}}{U_{be}} \quad (\text{definition of voltage gain})$$

$$A_P = \frac{P_{ki}}{P_{be}} = \frac{\left(\frac{U_{ki}^2}{R_{ki}}\right)}{\left(\frac{U_{be}^2}{R_{be}}\right)} = \frac{U_{ki}^2}{R_{ki}} \cdot \frac{R_{be}}{U_{be}^2} = \frac{U_{ki}^2}{U_{be}^2} \cdot \frac{R_{be}}{R_{ki}} = \left(\frac{U_{ki}}{U_{be}}\right)^2 \cdot \frac{R_{be}}{R_{ki}} = A_U^2 \cdot \underbrace{\frac{R_{be}}{R_{ki}}}_{R_{be} \approx R_{ki}} \approx A_U^2 \quad (\text{definition of power gain})$$

$$n_{dB} = 10n_B = \underbrace{10 \log A_P}_{R_{in} \approx R_{out}} \approx 20 \log A_U \quad (\text{definition of power gain level})$$

$$A_{U,NFB} = \frac{A_U}{1 + A_U \cdot \beta} \quad (\text{voltage gain with negative feedback})$$

## Solutions

1. a)  $U_1 = U_{source} \cdot \frac{R_1}{R_1 + R_2} = 230V \cdot \frac{2k\Omega}{2k\Omega + 20k\Omega} = 20.9V$   
b)  $A_U = \frac{U_{out}}{U_{in}} = \frac{20.9V}{230V} = 0.0909 = 9.09\%$   
c)  $A_P \approx A_U^2 = 0.0909^2 = 0.00826 = 0.826\%$   
d)  $n_{dB} = 10 \log A_P = 10 \log 0.00826 = -20.83dB = -2.083B$
2.  $\frac{U_1}{U_T} = \frac{R_1}{R_1 + R_2} \Rightarrow R_2 = R_1 \cdot \frac{U_T}{U_1} - R_1 = 1200\Omega \cdot \frac{1}{0.25} - 1200\Omega = 3600\Omega$
3. a)  $n_{dB} = 10 \log A_P \Rightarrow A_P = 10^{\frac{n_{dB}}{10}} = 10^{\frac{-23}{10}} = 0.005 = 0.5\%$   
b)  $A_P \approx A_U^2 \Rightarrow A_U \approx \sqrt{A_P} = \sqrt{0.005} = 0.0707 = 7.07\%$   
c)  $A_U = \frac{U_1}{U_T} = \frac{R_1}{R_1 + R_2} \Rightarrow R_2 = \frac{R_1}{A_U} - R_1 = \frac{1k\Omega}{0.0707} - 1k\Omega = 13.142k\Omega = 13142\Omega$
4.  $U_{out} = 85 V; A_U = 0.85$
5.  $U_{in} = 117.65 V; A_U = 0.85$
6.  $R_2 = 1867 \Omega$
7.  $R_1 = 343 \Omega$
8.  $R_1 = 105.3 \Omega$
9.  $R_2 = 46 k\Omega$
10. a) 20%  
b) 50%  
c) 100%  
d) 0%
11.  $U_{out} = 2 V$
12.  $n_{dB} \approx 20 \log A_U = 20 \log \frac{U_{out}}{U_{in}} = 20 \log 1000 = 60dB$
13. a)  $A_U \approx \sqrt{A_P} = \sqrt{1000} = 31.62$   
b)  $n_{dB} = 10 \log A_P = 10 \log 1000 = 30dB$
14.  $n_{dB} = 10 \log A_P \Rightarrow A_P = 10^{\frac{n_{dB}}{10}} = 10^{\frac{43}{10}} \approx 20000$
15.  $n_{dB} \approx 20 \log A_U = 20 \log 0.5 = -6.02dB$
16.  $n_{dB} \approx 20 \log A_U = 20 \log 2 = 6.02dB$

$$17. \quad n_{dB} = 10 \log A_P = 10 \log \frac{P_{out}}{P_{in}}$$

- a) 30 dB
- b) 17 dB
- c) 3 dB
- d) 0 dB
- e) -3 dB
- f) -10 dB
- g)  $-\infty$  dB

$$18. \quad n_{dB} = 10 \log A_P = 10 \log \frac{P_{out}}{P_{in}} \Rightarrow P_{out} = P_{in} \cdot 10^{\frac{n_{dB}}{10}}$$

- a) 500 kW
- b) 25 kW
- c) 50 W
- d) 6.3 W
- e) 5 W
- f) 3.97 W
- g) 0 W

$$19. \quad n_{dB} = 10 \log A_P = 10 \log \frac{P_{ki}}{P_{be}} \Rightarrow P_{ki} = P_{be} \cdot 10^{\frac{n_{dB}}{10}}$$

$$P_{ki,1} = P_{be} \cdot 10^{\frac{30}{10}} = P_{be} \cdot 1000$$

$$P_{ki,2} = P_{be} \cdot 10^{\frac{27}{10}} = P_{be} \cdot 501$$

$$\frac{P_{ki,1}}{P_{ki,2}} = \frac{P_{be} \cdot 1000}{P_{be} \cdot 501} \approx 2$$

$$20. \quad \frac{P_{ki,1}}{P_{ki,2}} = \frac{P_{be} \cdot 10^{\frac{50}{10}}}{P_{be} \cdot 10^{\frac{33}{10}}} = 10^{5-3,3} \approx 50$$

$$21. \quad n_{dB} \approx 20 \log A_U \Rightarrow A_U \approx 10^{\frac{n_{dB}}{20}} = 10^{\frac{50}{20}} = 316,23$$

$$A_{U,NVCS} = \frac{A_U}{1 + A_U \cdot \beta} = \frac{316,23}{1 + 316,23 \cdot 0,01} = 75,98$$

$$n_{dB} \approx 20 \log A_U = 20 \log 75,98 = 37,61 \text{ dB}$$

$$22. \quad n_{dB} \approx 20 \log A_U \Rightarrow A_U \approx 10^{\frac{n_{dB}}{20}}$$

$$A_U = 10^{\frac{13}{20}} = 4,4668$$

$$A_{U,NVCS} = 10^{\frac{10}{20}} = 3,1623$$

$$A_{U,NVCS} = \frac{A_U}{1 + A_U \cdot \beta} \Rightarrow \beta = \frac{1}{A_{U,NVCS}} - \frac{1}{A_U} = \frac{1}{3,1623} - \frac{1}{4,4668} = 0,0924$$

$$23. \quad A_{U,NVCS} = \frac{A_U}{1 + A_U \cdot \beta} \Rightarrow \beta = \frac{1}{A_{U,NVCS}} - \frac{1}{A_U} = \frac{1}{10^{\frac{20}{20}}} - \frac{1}{10^{\frac{26}{20}}} = 0,05$$

$$24. \quad \text{a) } n_{dB} \approx 20 \log A_U = 20 \log 100 = 40 dB$$

$$\text{b) } A_{U,NVCS} = \frac{A_U}{1 + A_U \cdot \beta} = \frac{100}{1 + 100 \cdot 0,05} = 25$$

$$\text{c) } n_{dB} \approx 20 \log A_U = 20 \log 25 = 28 dB$$