


# RC circuits

Dr. Rita Tünde Galántai

Department of Biophysics and Radiation Biology


06 October 2017

## Charging the RC circuit

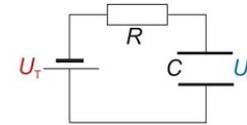

RC circuit: an electrical circuit consisting of an ohmic resistor and a capacitor (in series, in our case)

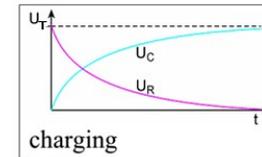Kirchhoff's voltage law (Kirchhoff's loop law, Kirchhoff's second law): as a result of conservation of energy, the directed sum (considering the signs) of voltages of electrical components along a loop within an electrical circuit is zero.



From Kirchhoff's 2<sup>nd</sup> law:  $U_T = U_R + U_C$

$$U_C = C \cdot q$$


$$U_C = U_T \cdot \left(1 - e^{-\frac{t}{RC}}\right)$$

$RC = \tau$  time constant

1

2

## Discharging the RC circuit

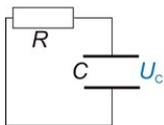



From Kirchhoff's 2<sup>nd</sup> law:

$$U_R + U_C = 0$$

$$U_C = -U_R$$

$$U_C = U_0 e^{-\frac{t}{RC}}$$

Note!  
Meaning of time constant:

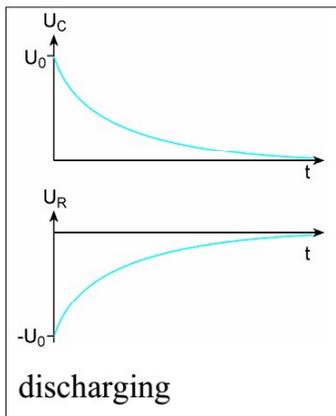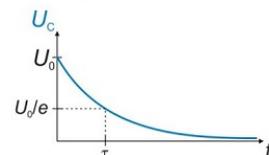

## Capacitor in alternating current circuits

**Alternating current circuit (AC circuit):** current and voltage changes periodically following a sine function:

$$I = I_{\max} \sin \omega t \quad \text{and} \quad U = U_{\max} \sin(\omega t + \varphi)$$

In an AC circuit the capacitor has a finite "resistance" called **capacitive reactance (symbol:  $X_C$ )**.

**Unit** of capacitive reactance:  $\Omega$  (ohm).

The alternating current keeps charging and discharging the capacitor, then again charging with the opposite polarity and again discharging and so forth.

$$X_C = \frac{1}{\omega C}$$

$\omega = 2\pi f$  is the angular frequency of the AC circuit

3


4

## Impedance

If an AC circuit contains both resistors and capacitors, the total "resistance" of the whole circuit is called **impedance**. Usual symbol:  $Z$ ; unit:  $\Omega$  (ohm).


Because of the phase shift between  $U$  and  $I$  in case of capacitors, the two quantities have to be considered perpendicular vectors which will define a right triangle: impedance will be related to the hypotenuse of this triangle.

### Impedance of a series RC circuit

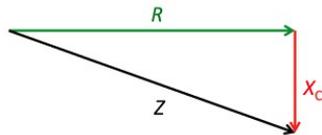

$$R^2 + (X_C)^2 = Z^2$$

### Impedance of a parallel RC circuit

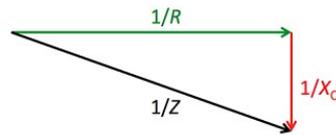

$$\left(\frac{1}{R}\right)^2 + \left(\frac{1}{X_C}\right)^2 = \left(\frac{1}{Z}\right)^2$$

Note! Pythagorean theorem:  $a^2 + b^2 = c^2$  (where  $c$  is the hypotenuse)


5

## Magnetism and Electromagnetic Induction

**Magnet:** a body with a special magnetic property

- **permanent magnets**  
special ores (early observation in ancient times near to *Magnesia*)  
Earth  
elementary particles of atom (electron, proton, neutron)

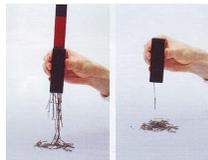- **non-permanent magnets**  
ferromagnetic materials (iron, cobalt, nickel)




Magnetic effect of electric current: moving charges induce magnetic field  
electromagnets

The strength of the magnet is given by the **magnetic moment**  
(Symbol:  $m$  or  $\mu$ )

7

## Natural magnets

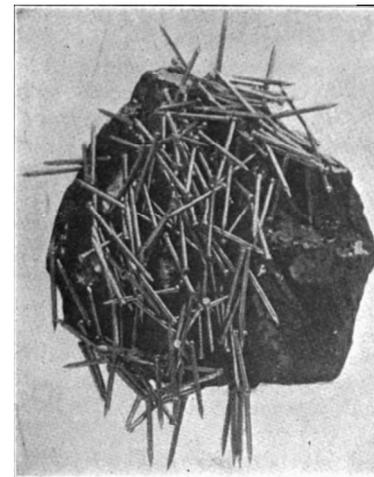


Lodestone



Magnetite ( $Fe_3O_4$ )

6

## Magnetic interaction

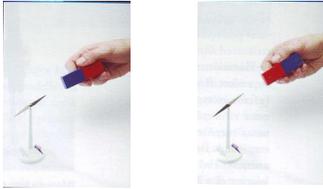

Electric phenomenon	Magnetic phenomenon
Two types of charges: positive and negative	Two types of poles: north pole and south pole
Like charges repel, the unlike charges attract each other	Like poles repel, the unlike pole attract each other
There are individual charges	There is no „one-polar” magnet (poles can not be separated)
Electric field	Magnetic field

9

## Magnetic field



Magnetic field of a magnet



Magnetic field of electric current flowing in a straight wire



Magnetic field of electric current flowing in an electromagnet

Strength of the magnetic field is characterized by:


**Magnetic flux density**

Symbol: B ; unit: T (tesla)

The structure, direction and strength of a magnetic field is visualized by **field lines**

10

## Magnetic field of the Earth

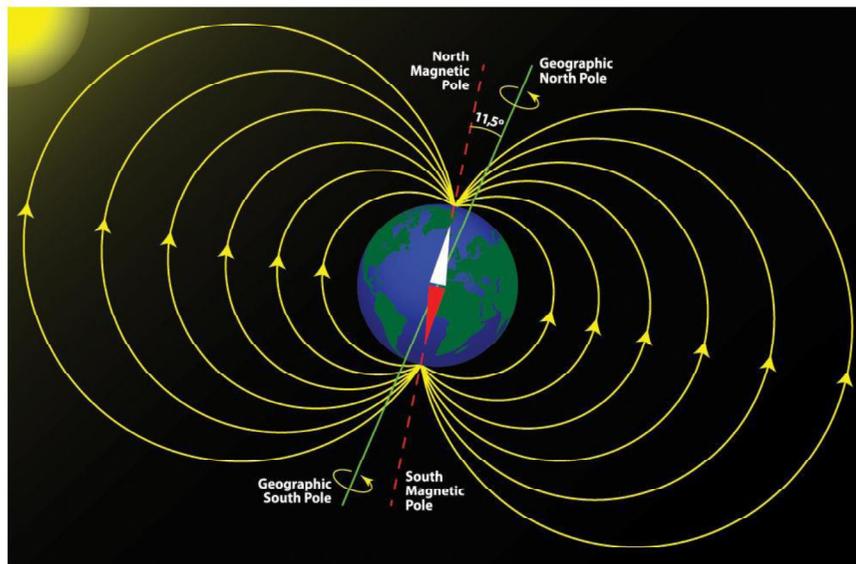

11

## Some examples...

Magnetic flux density of the Earth 0,03-0,06 mT  
 Magnetic flux density of fridge magnet ~ 10 mT

magnetic flux density used in MRI appliances 1-10 T

Generally:  
 Magnetic flux density of electromagnets:



$$B \sim N \cdot I$$

where **N** is the number of turns of the coil,  
**I** is the current intensity

12

## Magnetic Resonance Imaging (MRI)

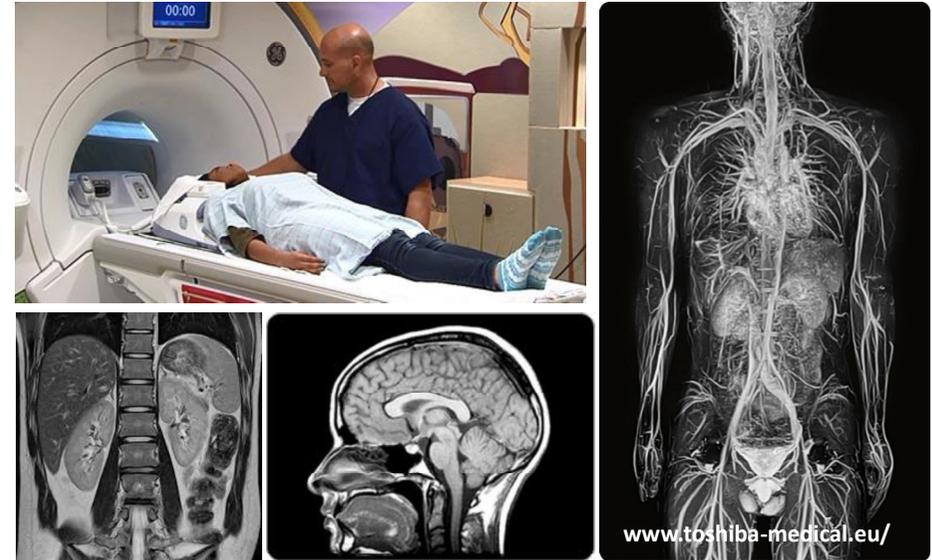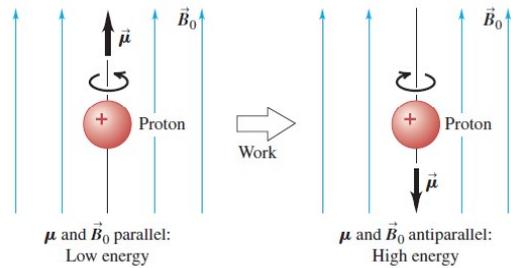
### Interaction between a magnet and an external magnetic fields



13

14

### Electromagnetic induction

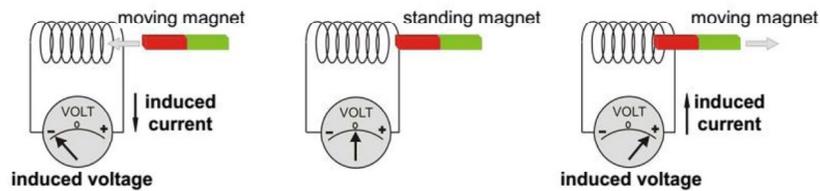


The magnetic field change caused by moving the magnet induces electric field, voltage, and current in the coil.

The faster the magnet moves, the higher the voltage.

**Lenz's law:** the induced voltage and current will act against the phenomenon creating it.

15

### Electromagnetic induction

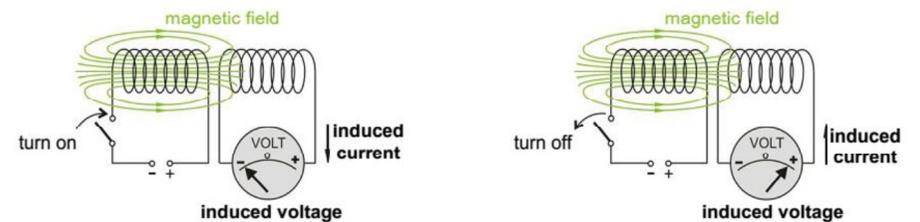

In the moment of switching the voltage source on or off the magnetic field changes: it will build up and break down, respectively.

During the change of the magnetic field, voltage is induced in the second coil.

Generally: the faster and greater the change in the magnetic field, the greater the induced voltage.


16

## Self-induction


**Self-induction:** induction of voltage in the same coil – or, in general, any kind of conductor – in which the current change causes change in the magnetic field.

Self-induction occurs any time a circuit is switched on or off.

### Lenz's law

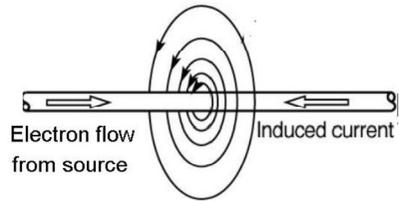

## LC circuit (resonant circuit)

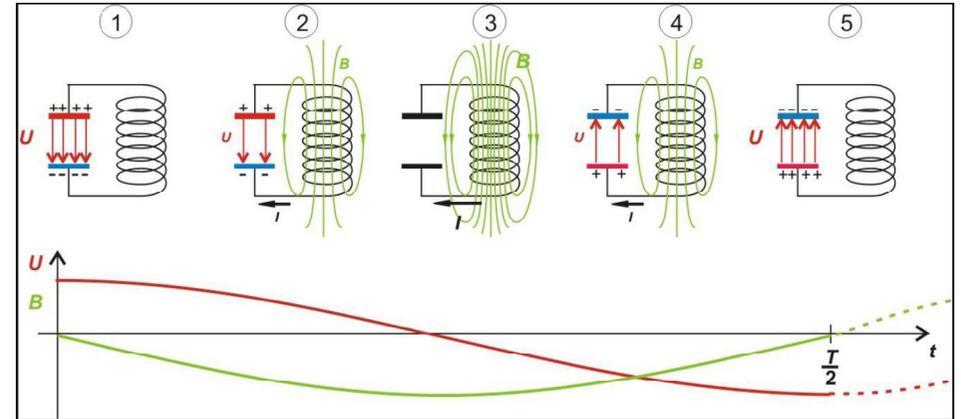

Electric and magnetic oscillations are going on linked to each other

↓  
electromagnetic oscillation