

## Electricity problems

1. How large is the resistance of a copper wire with 30 m length and  $1.5 \text{ mm}^2$  cross-section?  
 $\rho = 0.01786 \text{ } \Omega\text{mm}^2/\text{m}$  (0.357  $\Omega$ )
2. We connect 100  $\Omega$  resistance to 220 V voltage. How large is the current intensity in the circuit? (2.2 A)
3. We apply 20 V voltage to a circuit with 50 mS conductivity. How large is the current intensity in the circuit? (1 A)
4. We connect  $R_1 = 10 \text{ } \Omega$  and  $R_2 = 20 \text{ } \Omega$  resistances in parallel. There is 100 mA current intensity flowing through  $R_1$ . How large is the current intensity through  $R_2$ ? (50 mA)
5. We want to produce 1 V output voltage with a voltage divider. The input voltage is 20 V. The upper part of the resistance divider has 19 k $\Omega$  resistance. How large should be the resistance of the lower part? (1 k $\Omega$ )
6. The resistance of 10 k $\Omega$  can dissipate 0.5 W power without any destruction. How large is the highest voltage that can be connected to it? (70.7 V)
7. In a given point of the electric field there is a probe with 0.01 mC charge. A force of 0.02 N acts on the probe. What is the electric field strength in this point? (2000 V/m)
8. A capacitor consists of two aluminum plates of  $100 \text{ cm}^2$  surface. Their distance is 0.5 mm. The dielectric is air ( $\epsilon = 8.85 \cdot 10^{-12} \text{ F/m}$ ). How large is the capacity of the capacitor? (177 pF)
9. We connect  $C_1 = 200 \text{ pF}$ ,  $C_2 = 400 \text{ pF}$  and  $C_3 = 400 \text{ pF}$  capacitors in series. How large is the equivalent capacity? (100 pF)
10. We need an electromagnet with 1 T magnetic induction. The surface area of magnetic poles is  $1 \text{ cm}^2$ , their distance is 2 mm. How large magnetic flux should be produced by the coil? (0.0001 Wb)
11. The length of the spark produced by a piezoelectric gas-lighter is 5 mm. How high voltage should be produced by the piezo-crystal to get spark in dry air. The breakdown resistance of dry air is 3000 V/mm. (15 kV)
12. The thickness of a cell membrane is 5 nm. The resting potential of the membrane is 90 mV. How large is the electric field strength in the membrane? (18 MV/m)